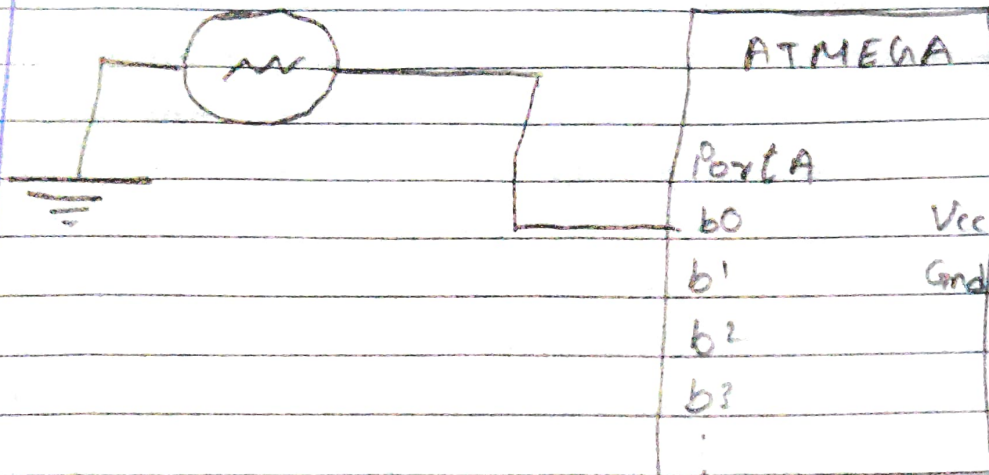


→ Circuit diagram for Question 1, 2, 3



→ Circuit diagram for Question 4, 5

