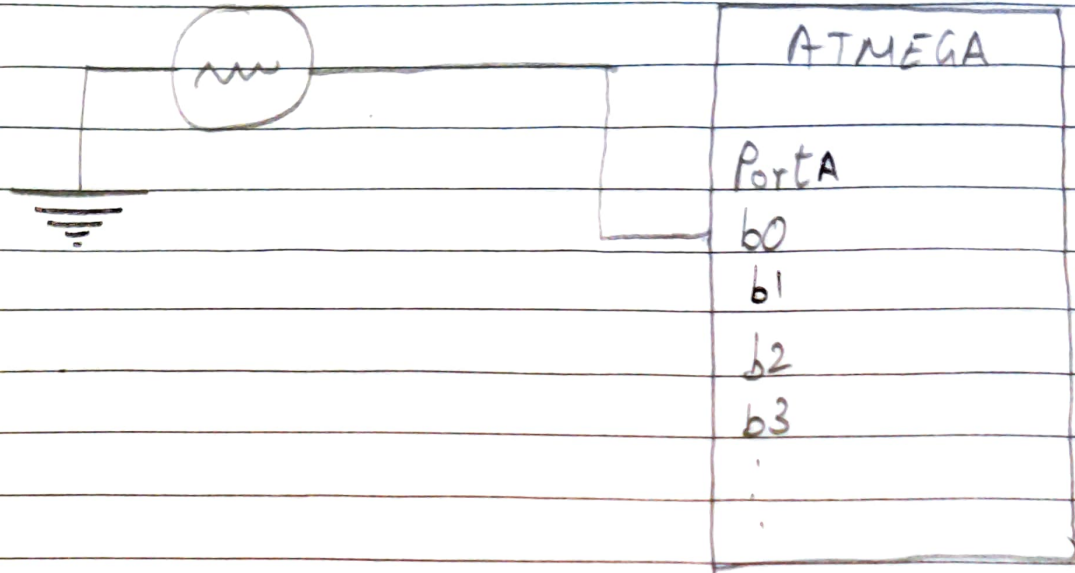


→ Circuit diagram for Question 1a, 1b, 2



→ Circuit Diagram for Question 3

